
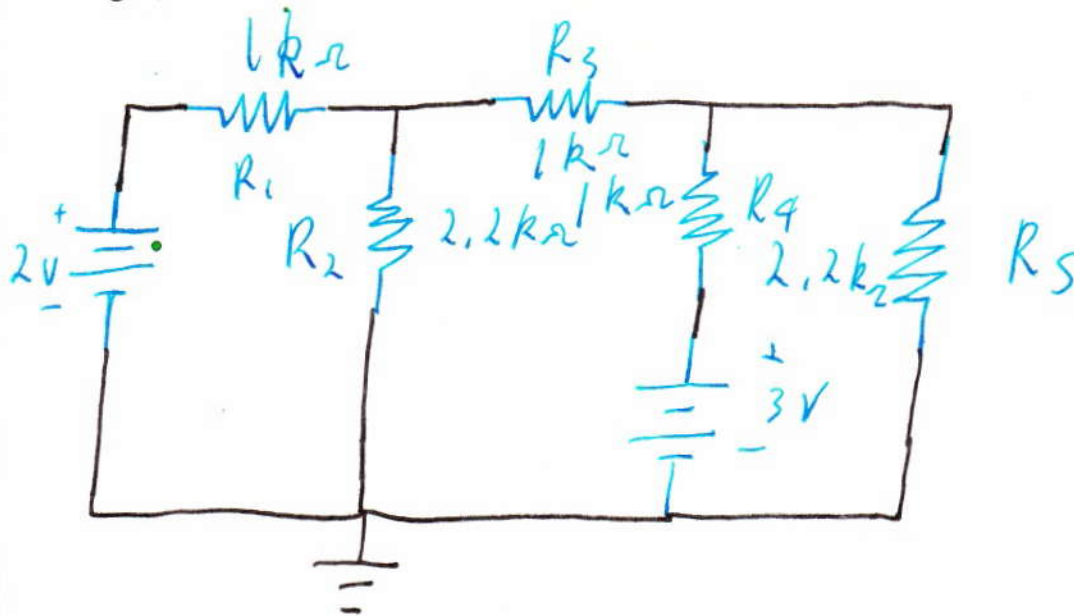


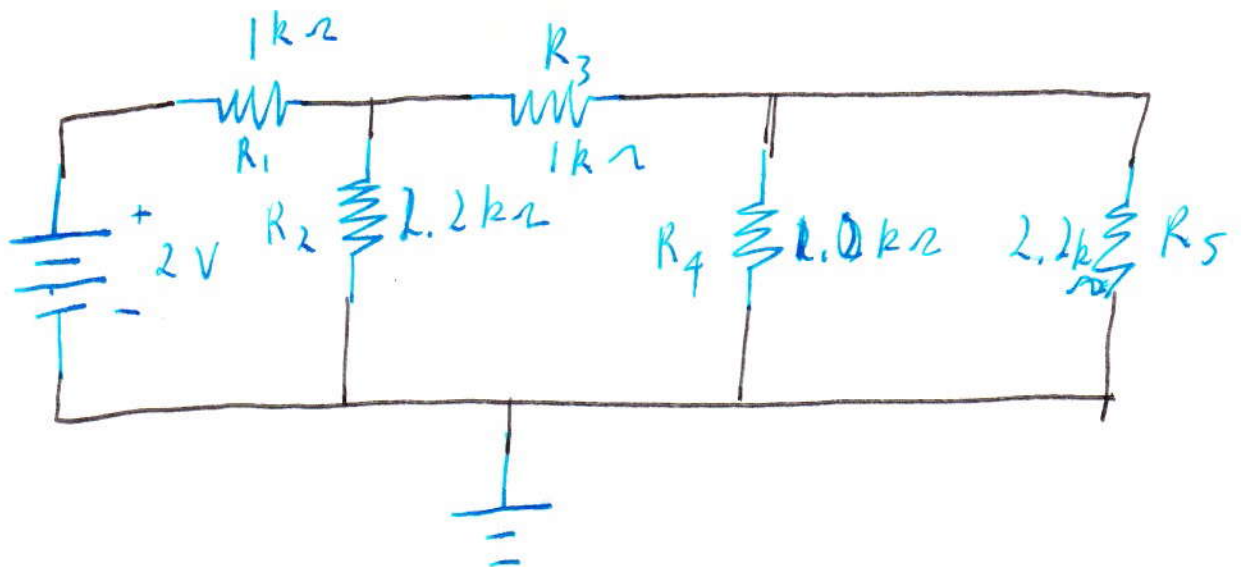7) Using the Superposition method, calculate the current through  $R_5$ .



Step 1 make circuits independent of each source. Short all <sup>other</sup> voltage sources and break current sources.

Superposition circuit 1. 2V source  
 first objective Thevenin circuit  
 for initial current



$R_{Th}$  combining resistors

$$\frac{10^3 \times 2.2 \times 10^3}{3.2 \times 10^3} = R_{4||5} = 687.5 \Omega$$

$$R_{4||5} + R_3 = 687.5 + 1000 = 1687.5 \Omega$$

$$R_{3+4||5} = 1687.5 \Omega$$



$$R_2 || R_{3+4||5} = \frac{1687.5 \times 2.2 \times 10^3}{3887.5} = 959.98 \Omega$$

$$R_{th} = R_1 + R_{2||((3+4)||5)} = 1954.983 \Omega$$

$$R_{Th} = 1954.983 \Omega$$

$$V = iR$$
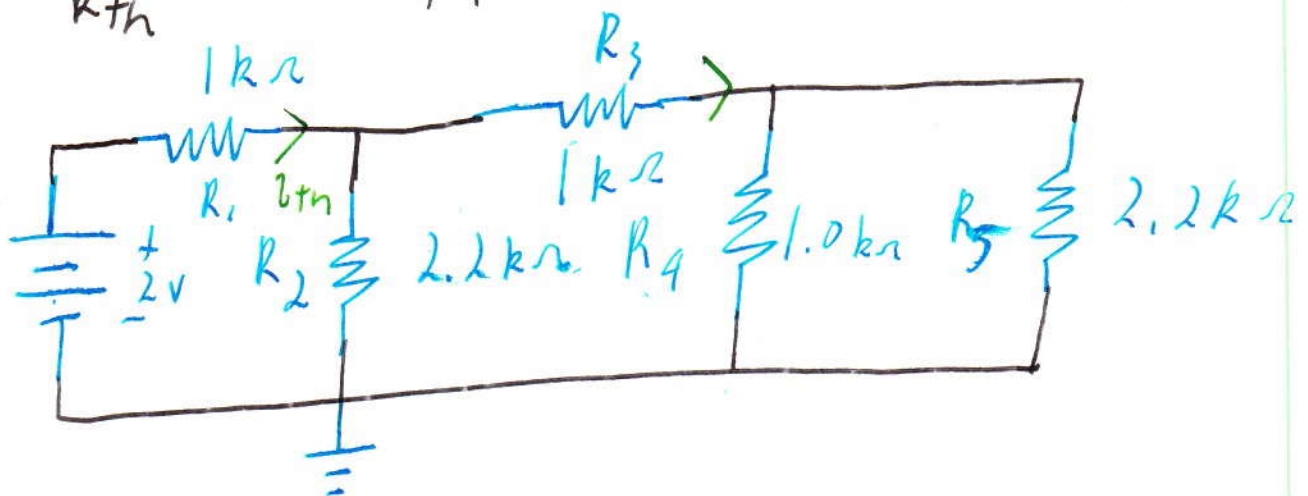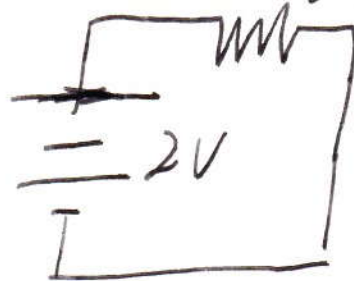
$$\frac{V_{th}}{R_{th}} = i \quad i_{th} = 1.023 \text{ mA}$$



objective is  $i_{R5}$

current divider

$$\frac{R_{other}}{\sum R} i_s = i_{Target}$$

$$R_{3+(4115)} = 1687.5 \Omega$$

$$R_2 = 2.2 \times 10^3 \Omega$$

$$i_{R_3} = \frac{2.2 \times 10^{-3}}{3887.5} \quad 1.023 \times 10^{-3}$$

$$0.579 \text{ mA} = i_{R_3}$$

Current divider again

$$\frac{R_{\text{other}}}{\Sigma R} i_{\text{source}} = i_{\text{target}}$$


$$\frac{\cancel{10^3}}{3.2 \times \cancel{10^3}} \quad 0.579 \times 10^{-3}$$

$$1.809 \times 10^{-4}$$

$$\cancel{0.180 \times 10^{-1}}$$


$$0.180 \text{ mA} = i_{R_S} \quad V_S = 2$$

Superposition circuit 2  $V = 3V$

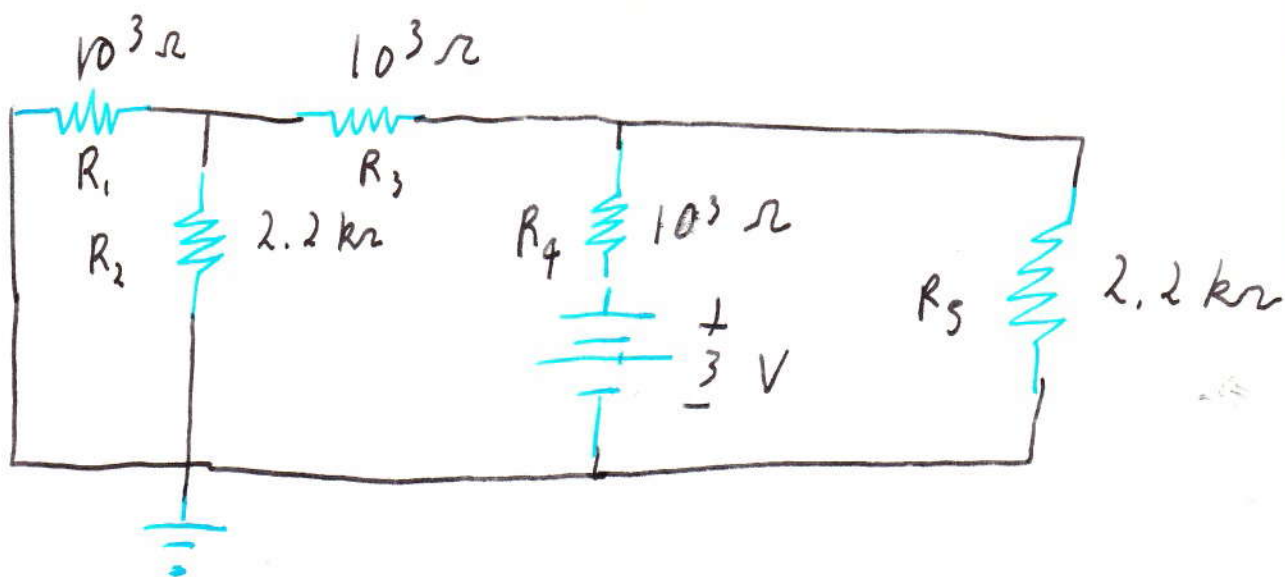

$$R_{1||2} = \frac{2.2 \times 10^3 \times 10^3}{3.2 \times 10^3} \quad R_{(1||2)+3} = 1687.5 \Omega$$

$$R_{1||2} = 687.5 \Omega$$

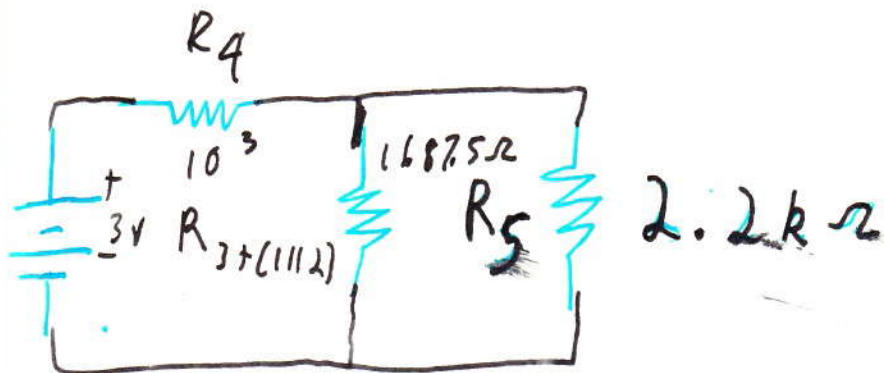

$$R_{(3+(1112))||5} = \frac{1.687.5 \times 2.2 \times 10^3}{1687.5 + 2.2 \times 10^3}$$

$$R_{(3+(1112))||5} = \frac{3712.5 \times 10^3}{3887.5}$$



$$R_{3+(1112)||5} = 954.983 \Omega$$

$$R_{Th} = 1954.983 = R_{4+(3+(1112))||5}$$

$$\frac{V_{Th}}{R_{Th}} = i_{Th}$$

$$i_s = 1.534 \text{ mA}$$



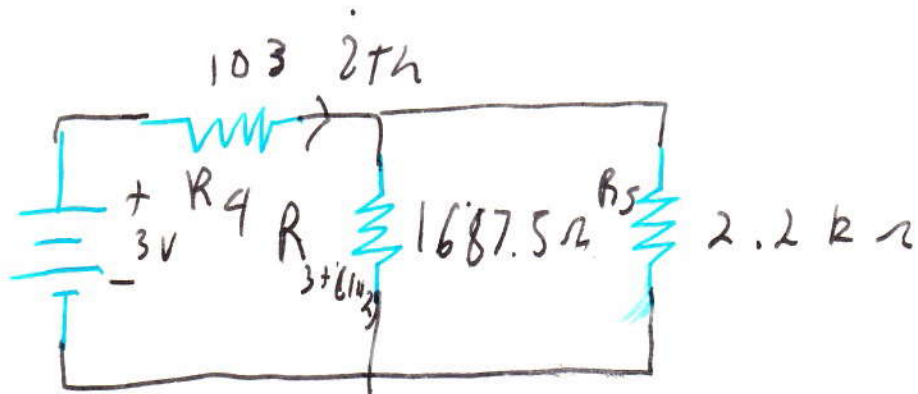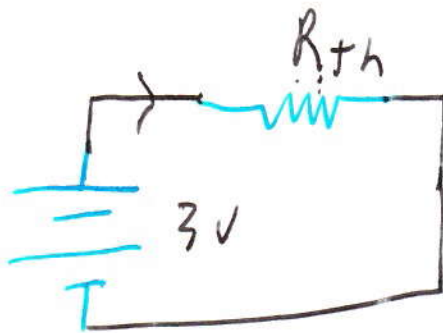

Current divider

$$\frac{R_{other}}{\sum R} i_S = i_{Target}$$

$$\frac{1687.5}{3887.5} i_S = 1.534 \text{ mA}$$

$$i_{R_S \text{ @ } V_S=3} = 0.665 \text{ mA}$$




$$i_{R_S - V_S = 2} + i_{R_S - V_S = 3} = i_{R_S}$$

$$i_{R_S} = 0.579 \times 10^{-3} + 0.665 \times 10^{-3} \text{ mA}$$

$$i_{R_S} = 1.244 \text{ mA}$$


Superposition circuit 2  $V = 3V$

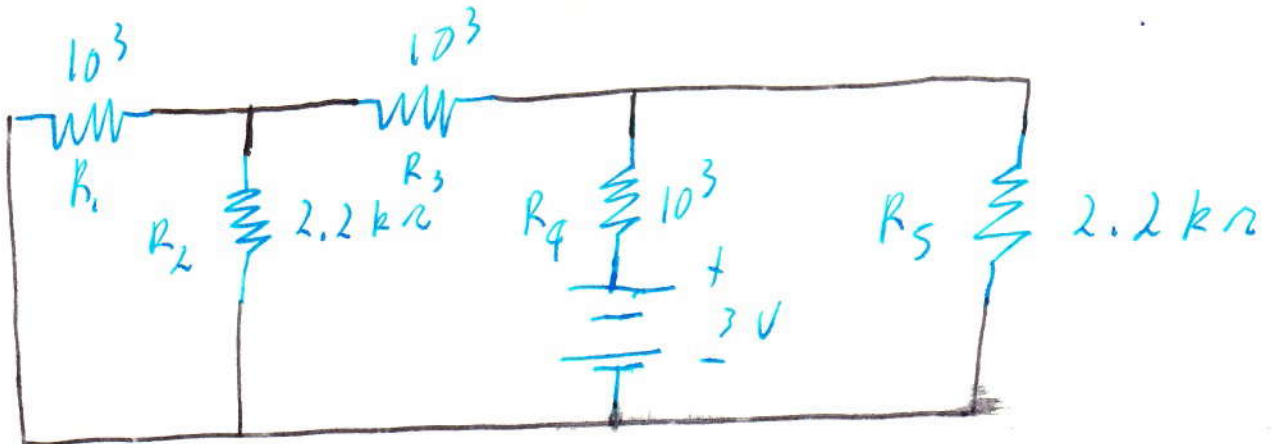

$$R_{1||2} = \frac{2.2 \times 10^3 \times 10^3}{3.2 \times 10^3}$$

$$R_{1||2} = 687.5 \Omega$$

$$R_{(1||2)+3} = 1687.5 \Omega$$

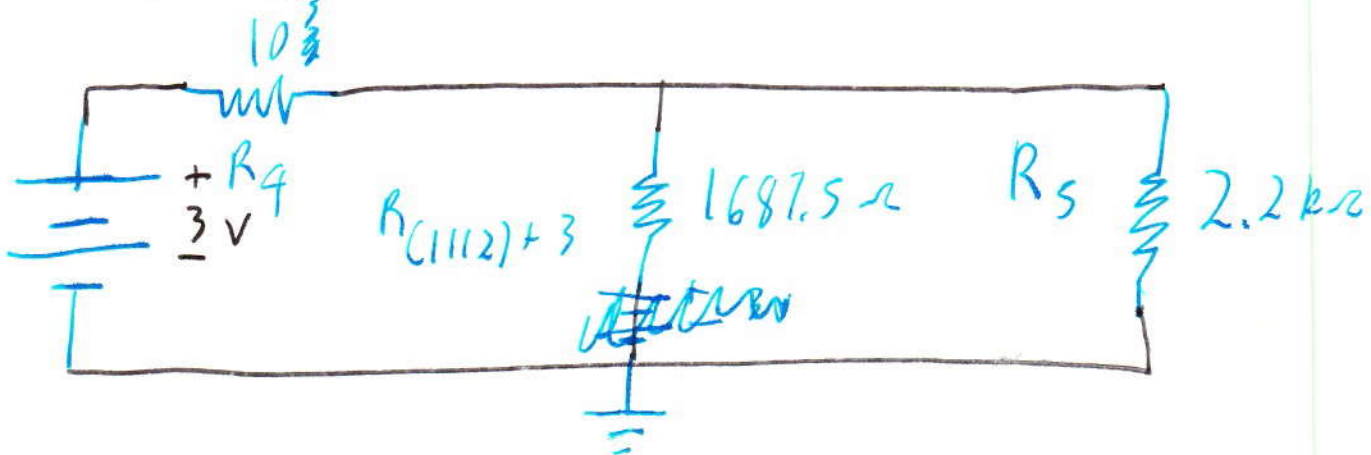

$$\dot{I}_{R5-V5=2} + \dot{I}_{R5-V5=3} = \dot{I}_{R5}$$

$$\dot{I}_{R5} = 0.665 \times 10^{-3} + 0.579 \times 10^{-3} \text{ A}$$

7 alternate)

attempting source transformation


$$V = iR$$

$$\frac{V}{R} \cdot i = \frac{2}{10^3}$$

$$\frac{V}{R} = \frac{3}{2.2 \times 10^3}$$

$$i = 2 \text{ mA}$$

$$i = 1.363 \text{ mA}$$

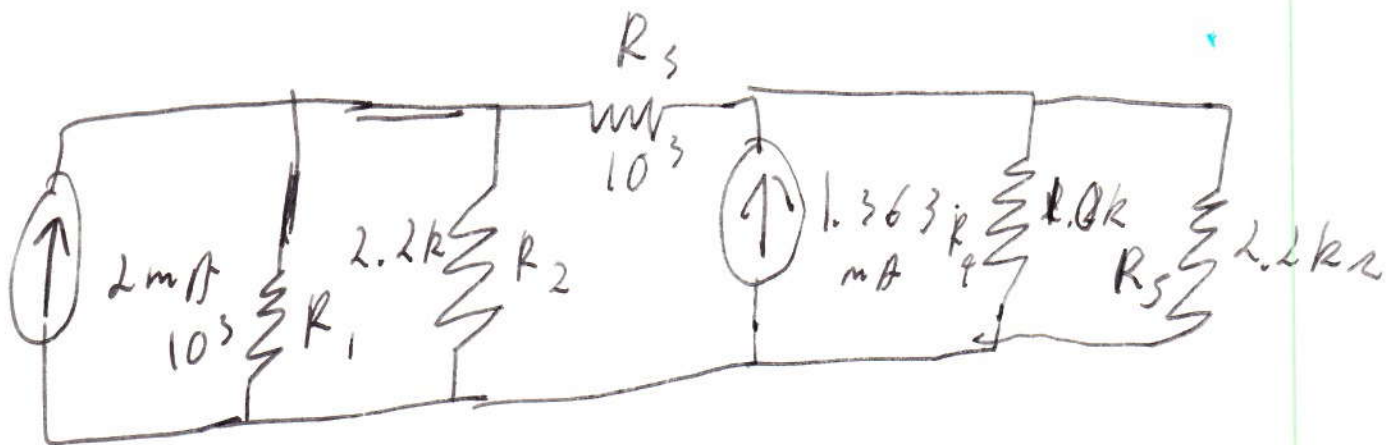


$$R_{1||2} = 687.5$$

~~R1~~

$$\frac{V}{R} = i$$



$$V = iR$$

$$V = 1.375 \text{ V}$$

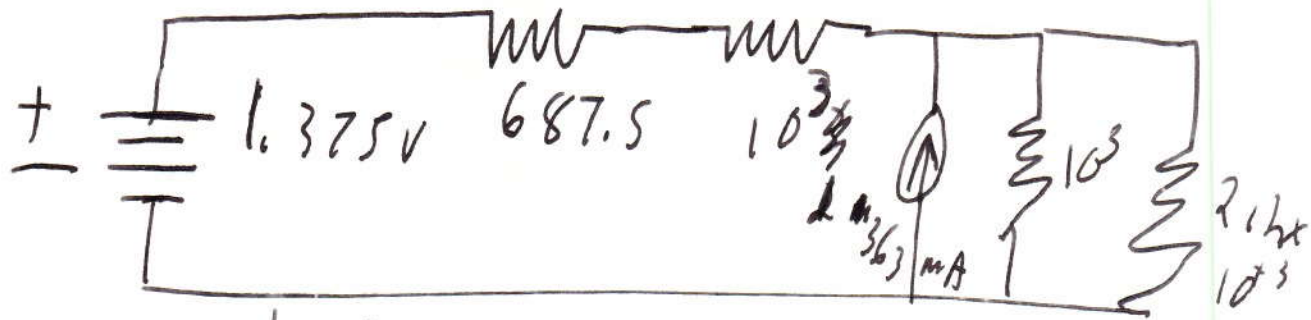



$$\frac{1.375}{1687.5} \approx 0$$

$$8.148 \times 10^{-4}$$

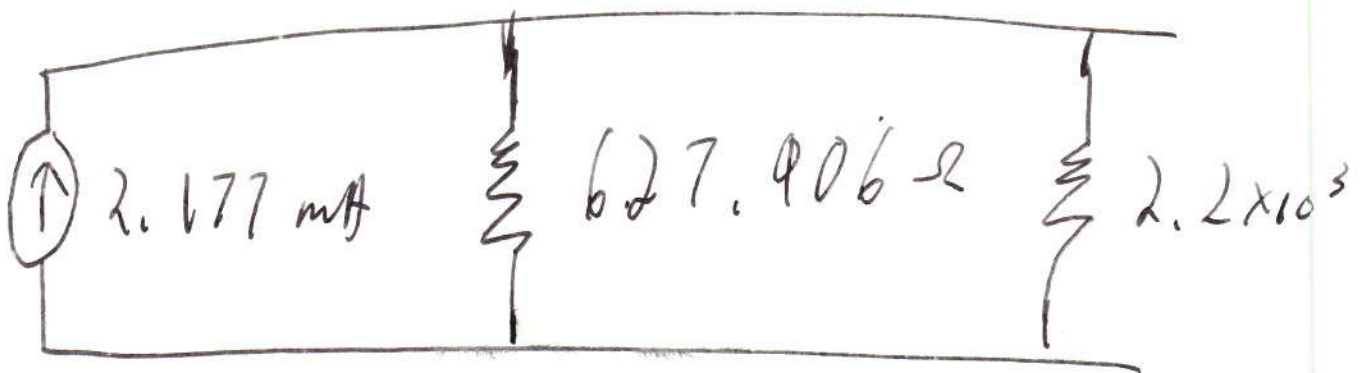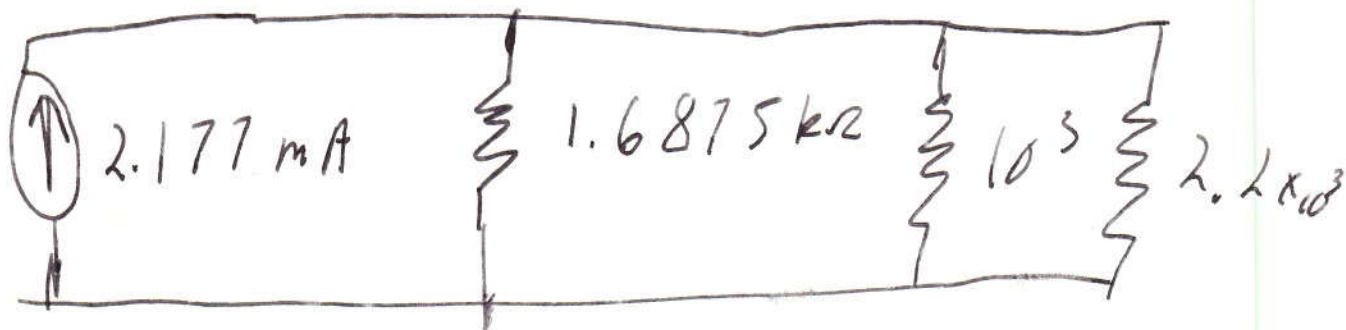

$$V = iR$$

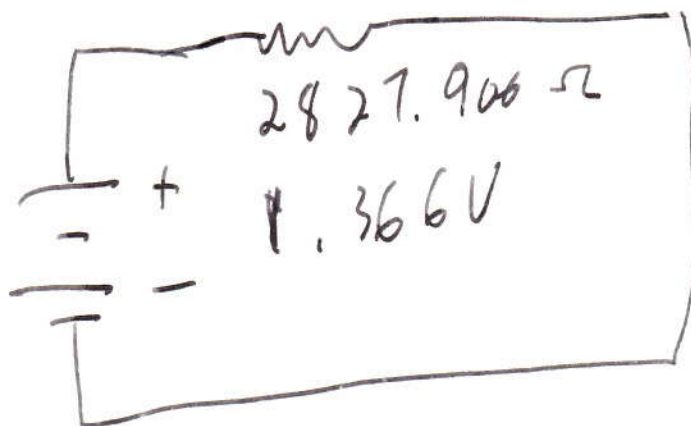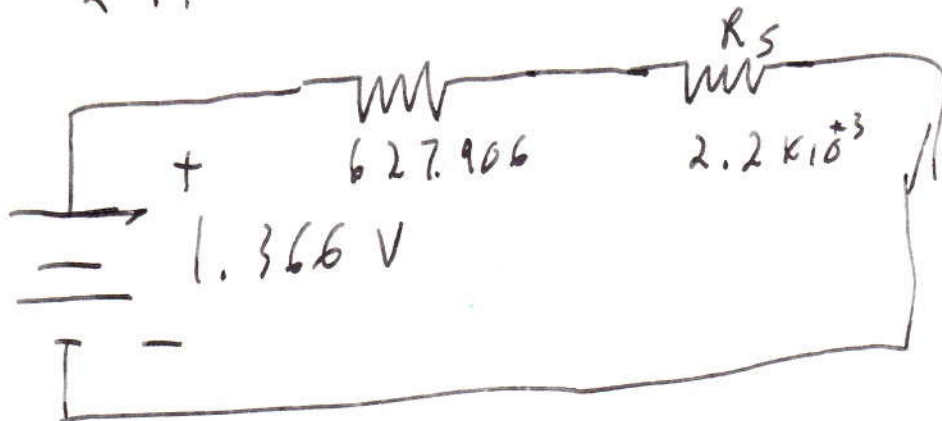
$$2.177 \times 10^{-3} \times 627.906 \approx 1.366 \text{ V}$$



$$i_{R_S} = 4.830 \times 10^{-4}$$

$$i_{R_S} = 0.483 \text{ mA}$$

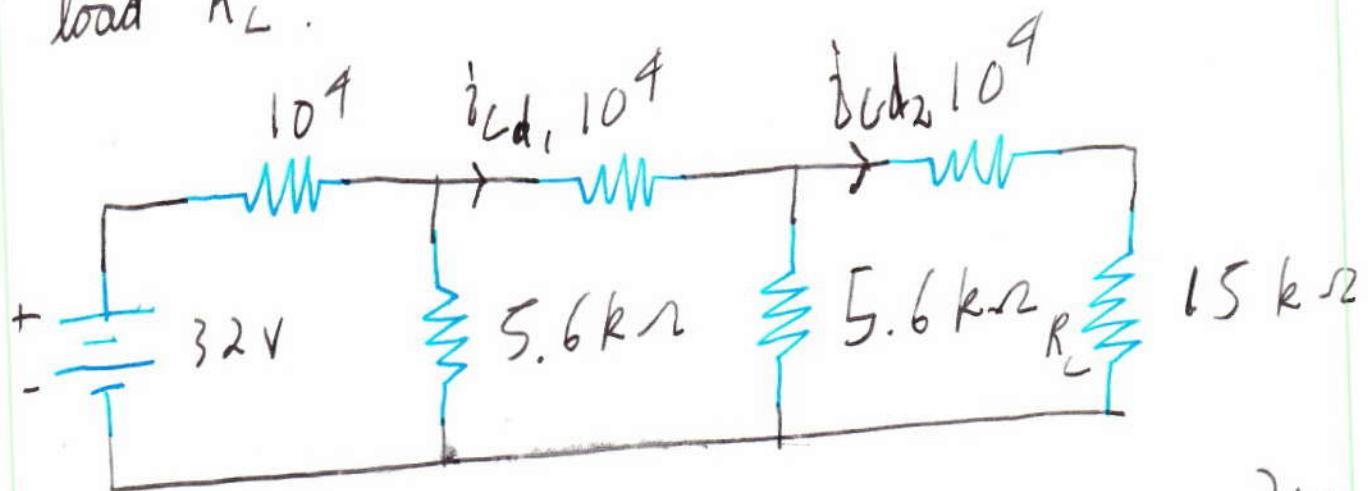19) Using Thevenin's theorem, determine the current through the load  $R_L$ .



$$\left( (10^4 + 15 \times 10^3) \parallel 5.6 \text{ k}\Omega \right) + 10^4 \parallel 5.6 \text{ k}\Omega + 10^4$$


$$25000 \parallel 5.6 \text{ k}\Omega = 4575.163 \Omega$$

$$4575.163 + 10^4 = 14575.163 \Omega$$

$$14575.163 \parallel 5.6 \times 10^3 = 4045.613 \Omega$$

$$4045.613 + 10^4 = 14045.613 \Omega$$



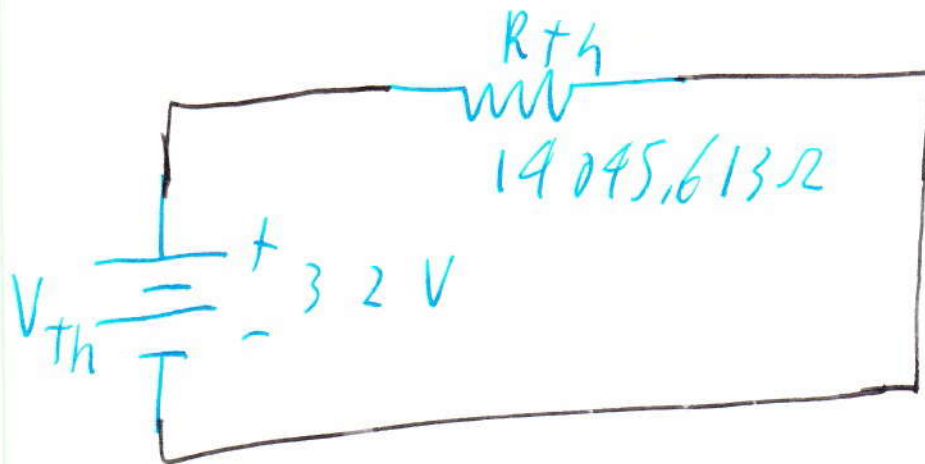

~~V~~  
V

$$V = iR$$

$$\frac{V_{th}}{R_{th}} = i_{th}$$

$$\frac{32}{14045.613} = 2.278 \text{ mA} = i_{th}$$

Current divider

$$i_T = \frac{R_{other}}{\sum R} i_g$$

$$\frac{5.6 \text{ k}}{5.6 \text{ k} + 14575.163} \times 2.278 \text{ mA}$$


$$6.314 \times 10^{-4} \text{ A} = i_{Cd1}$$

$$i_{Cd2} = \frac{5.6 \text{ k}}{5.6 \text{ k} + 25000} \times 6.314 \times 10^{-4}$$

$$i_{Cd2} = 1.155 \times 10^{-4}$$

$$i_{RL} = 0.115 \text{ mA}$$

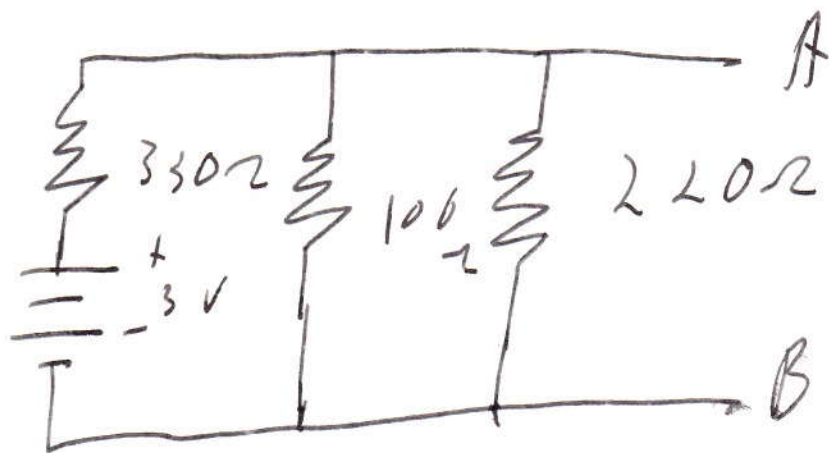31) apply Norton's theorem to the circuit



$$V = iR$$

$$\frac{V}{R} = i$$


$$\frac{3}{330}$$

$$\frac{1}{110} = i$$


$$i = 9.090 \text{ mA}$$

$$\frac{1}{\frac{1}{330} + \frac{1}{100} + \frac{1}{220}} = R_{11}$$

$$R_{11} = 56.896 \Omega$$

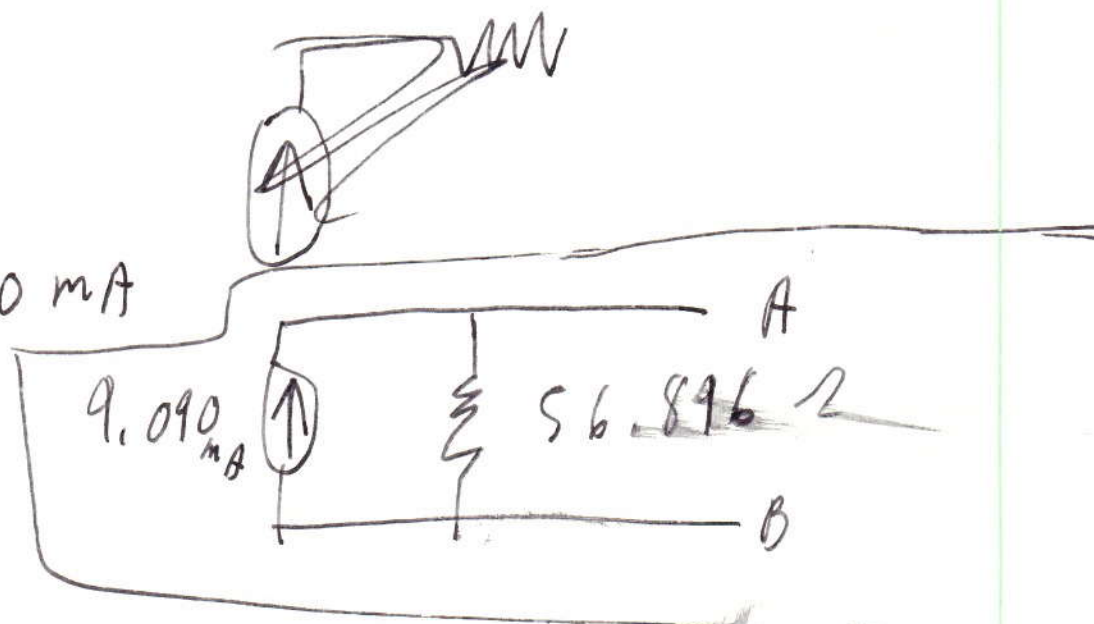

33) Determine  $R_L$  for maximum power.

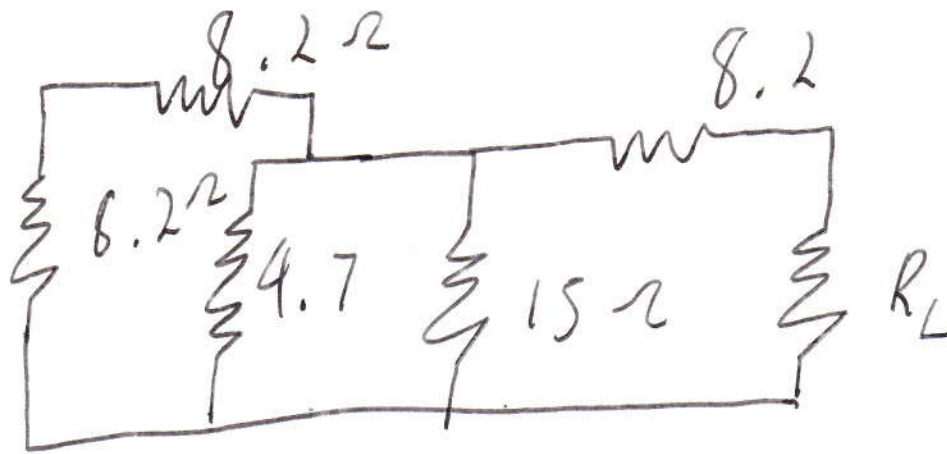


$$(6.2 \parallel 4.7 \parallel 15) + 8.2$$

$$2.937\ \Omega + 8.2 = 11.137\ \Omega$$


For max power transfer  $R_L =$

$$R_{\text{internal}}, \text{ so } \boxed{11.137\ \Omega = R_L}$$

37/a)

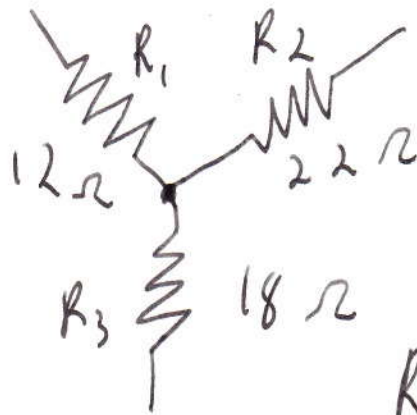
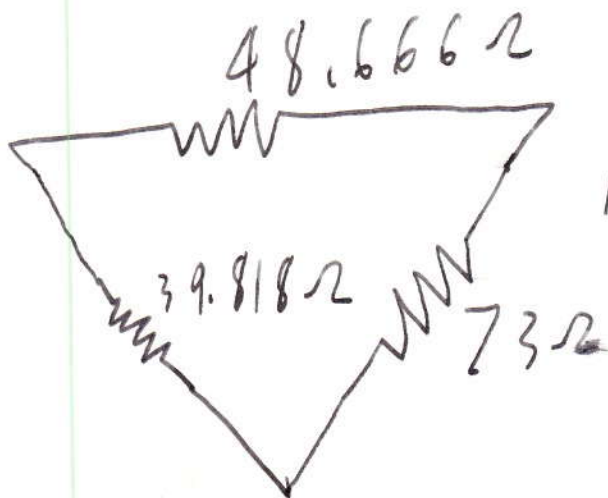
$$\frac{R_1 R_2 + R_2 R_3 + R_1 R_3}{R_{\text{opposite}}}$$



$$\text{numerator} = 876\ \Omega$$

$$\frac{876}{22} = 39.818\ \Omega$$

$$\frac{876}{18} = 48.666\ \Omega$$


$$\frac{876}{12} = 73\ \Omega$$

b)

$$\frac{R_1 R_3 + R_2 R_3 + R_2 R_1}{R_{\text{opposite}}}$$

Numerator  $6.8k \times 4.7k + 3.3k \times 4.7k + 3.3k \times 6.8k$

Numerator  $= 6.991 \times 10^7 \Omega$

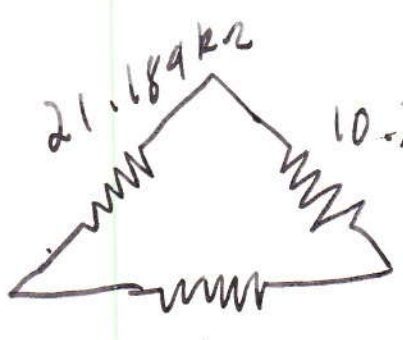

$$\frac{6.991 \times 10^7}{6.8k} = 10.280k\Omega$$

$$\frac{6.991 \times 10^7}{3.3k} = 21.189k\Omega$$

$$\frac{6.991 \times 10^7}{4.7k} = 14.874k\Omega$$