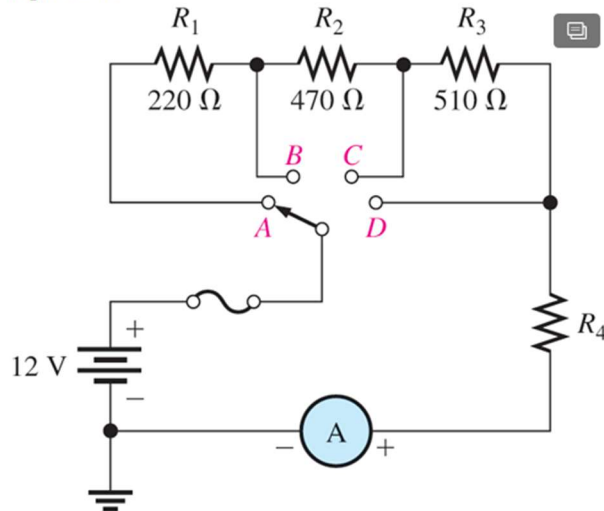


CPE 1140 - Homework # 5

Chapter 5

25. For the circuit in [Figure 5-73](#) the meter reads 7.84 mA when the switch is in position *A*.
- What is the resistance of R_4 ?
 - What should be the meter reading for switch positions *B*, *C*, and *D*?
 - Will a $\frac{1}{4}$ A fuse blow in any position of the switch?

Figure 5-73



A)

$$V = IR$$

$$\frac{V}{I} = R_{\text{series}}$$

$$\frac{12}{7.84 \times 10^{-3}} = 1530.612 \Omega = R_{\text{series}}$$

$$R_{\text{series}} = R_1 + R_2 + R_3 + R_4$$

$$R_{\text{series}} = 220 \Omega + 470 \Omega + 510 \Omega + R_4$$

$$R_{\text{known}} = 1200 \Omega$$

$$R_{\text{series}} - R_{\text{known}} = R_4$$

$$1530.612 - 1200 = 330.612 \Omega$$

$$R_4 = 330 \Omega$$

Truncated due to the nearest real resistor.

B)

$$R_{\text{series}} - R_1 = R_{\text{position B}}$$

$$1530 \, \Omega - 220 \, \Omega = 1310 \, \Omega$$

$$R_{\text{position B}} = 1310 \, \Omega$$

$$\frac{V}{R} = I$$

$$\frac{12}{1310} = 9.160 \, \text{mA}$$

$$R_{\text{position C}} = R_{\text{series}} - R_1 - R_2$$

$$R_{\text{position C}} = 1530 \, \Omega - 220 \, \Omega - 470 \, \Omega$$

$$R_{\text{position C}} = 840 \, \Omega$$

$$\frac{V}{R} = I$$

$$\frac{12}{840} = 14.285 \, \text{mA}$$

$$R_{\text{position D}} = 330 \, \Omega$$

$$\frac{V}{R} = I$$

$$\frac{12}{330} = 36.363 \, \text{mA}$$


c)

$$\frac{1}{4} * 1000 = 250 \text{ mA}$$

All the positions are under 250 mA. Therefore, the circuit should be safe in all positions.

41. Determine the voltage with respect to ground for output A , B , and C in Figure 5–83(a).

Figure 5–83

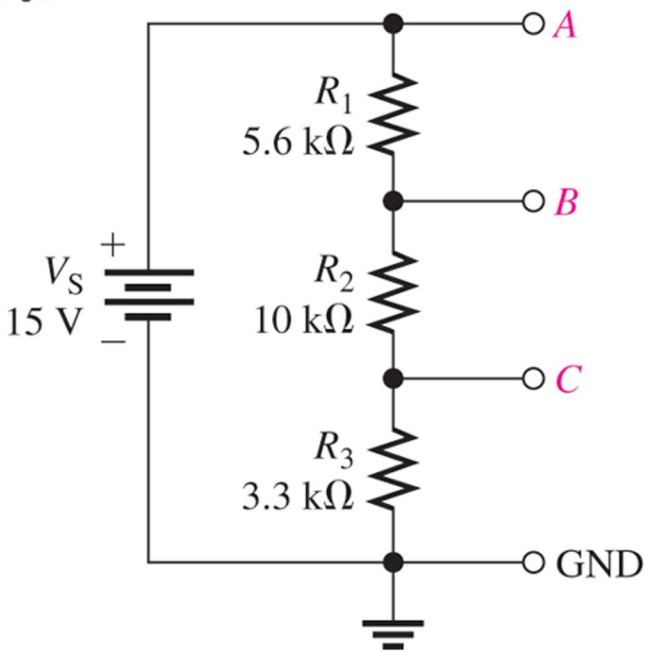

(a)

$$R_{\text{series}} = (5.6 + 10 + 3.3) \times 10^3$$

$$R_{\text{series}} = 18.9 \text{ k}\Omega$$

$$\text{Voltage divider} = V_{\text{source}} * \frac{R_{\text{target resistors}}}{R_{\text{series}}}$$

$$V_{A-\text{Ground}} = 15\text{V} \text{ It gets all the voltage}$$

$$V_{B-\text{Ground}} = 15\text{V} * \frac{13.3}{18.9}$$

$$V_{B-\text{Ground}} = 10.555 \text{ V}$$

$$V_{C-\text{Ground}} = 15\text{V} * \frac{3.3}{18.9}$$

$$V_{C-\text{Ground}} = 2.619 \text{ V}$$

49. If you double the voltage across a resistor, by how much does the power increase?

$$V = IR$$

$$\frac{V}{R} = I$$

$$P = IV$$

$$P = \frac{V^2}{R}$$

four times.