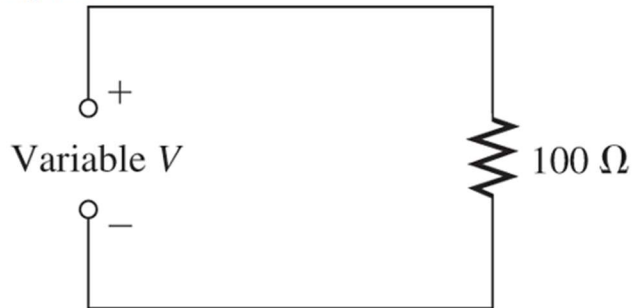


EET/CPE 1140 - Homework # 3

Chapter 3


5. A variable voltage source is connected to the circuit of [Figure 3–21](#). Start at 0 V and increase the voltage in 10 V steps up to 100 V. Determine the current at each voltage point, and plot a graph of V versus I . Is the graph a straight line? What does the graph indicate?

Figure 3–21



Computed in a table in next page

Voltage[V] {Volts} (Control variable) Resistance [R] {Ohms} (constant) = 100Ω $\frac{V}{R} = I$	Current[I] {Amperes} (Dependent variable or output variable)
$\frac{0}{100}$	0.000
$\frac{10}{100}$	0.100
$\frac{20}{100}$	0.200
$\frac{30}{100}$	0.300
$\frac{40}{100}$	0.400
$\frac{50}{100}$	0.500
$\frac{60}{100}$	0.600
$\frac{70}{100}$	0.700
$\frac{80}{100}$	0.800
$\frac{90}{100}$	0.900
$\frac{100}{100}$	1.000

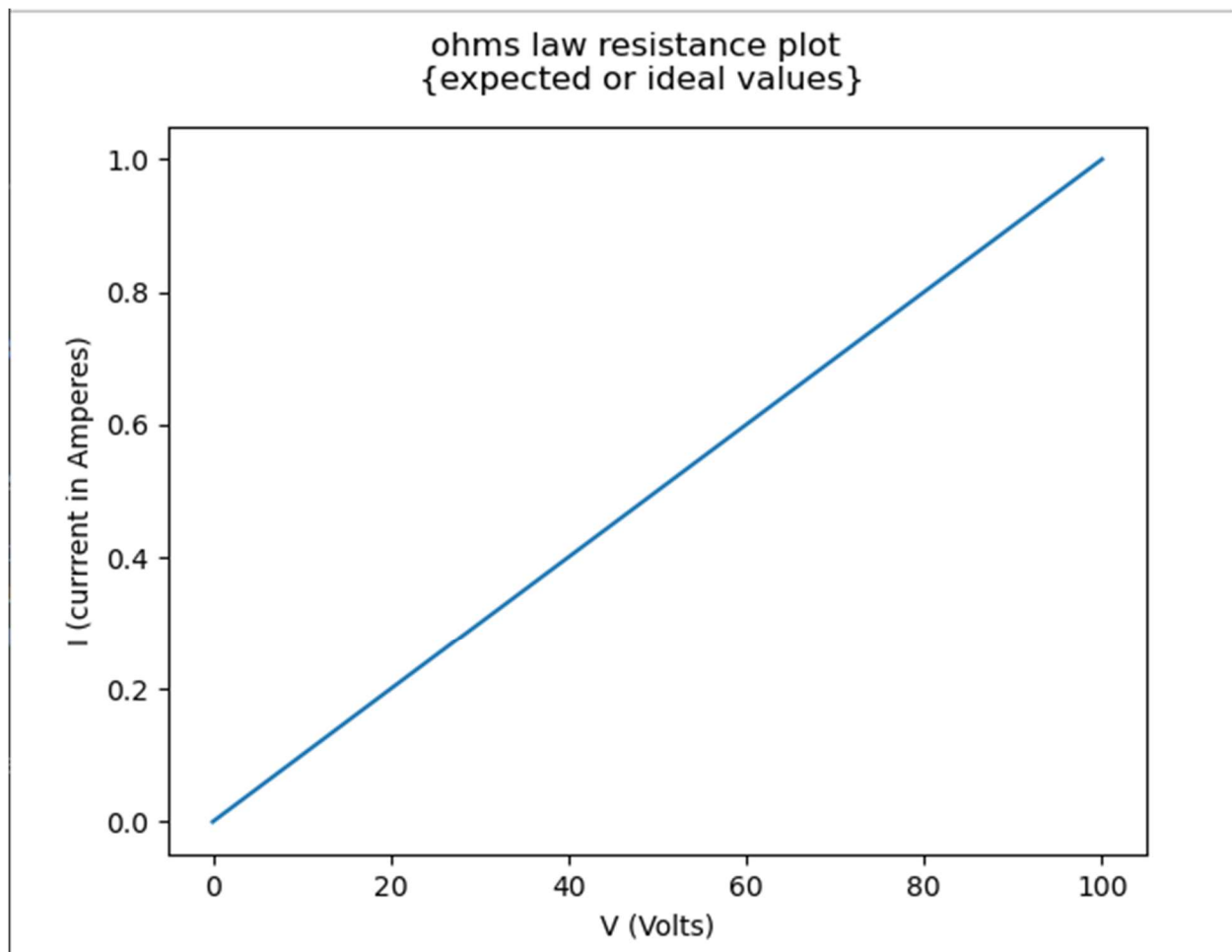

Plot made with matplotlib.lib in python included code.

```
import matplotlib.pyplot as ohms_law

#initialization of variables
current_output_data = [] # y output
resistance = 100.0 # resistance in ohms constant
voltage = [] # x control variable
temp = 0.0 # computations output temporary variable

# voltage initialization 0-100 in increments of 10
# some excess in temp but not pushed to the list
for i in range(11):
    voltage.append(temp)
    temp += 10.0
# computes current value using ohms law  $V/R = I$ 
for k in range(len(voltage)):
    current_output_data.append(voltage[k]/resistance)

# X label data first in a list

ohms_law.plot(voltage,current_output_data)

# labels section
```

```
ohms_law.suptitle("ohms law resistance plot \n{expected or ideal  
values}")
```

```
ohms_law.ylabel("I (current in Amperes)")
```


```
ohms_law.xlabel("V (Volts)")
```

```
#displays the graph
```

```
ohms_law.show()
```

7. Figure 3–22 is a graph of current versus voltage for three resistance values. Determine R_1 , R_2 , and R_3 .

Figure 3–22

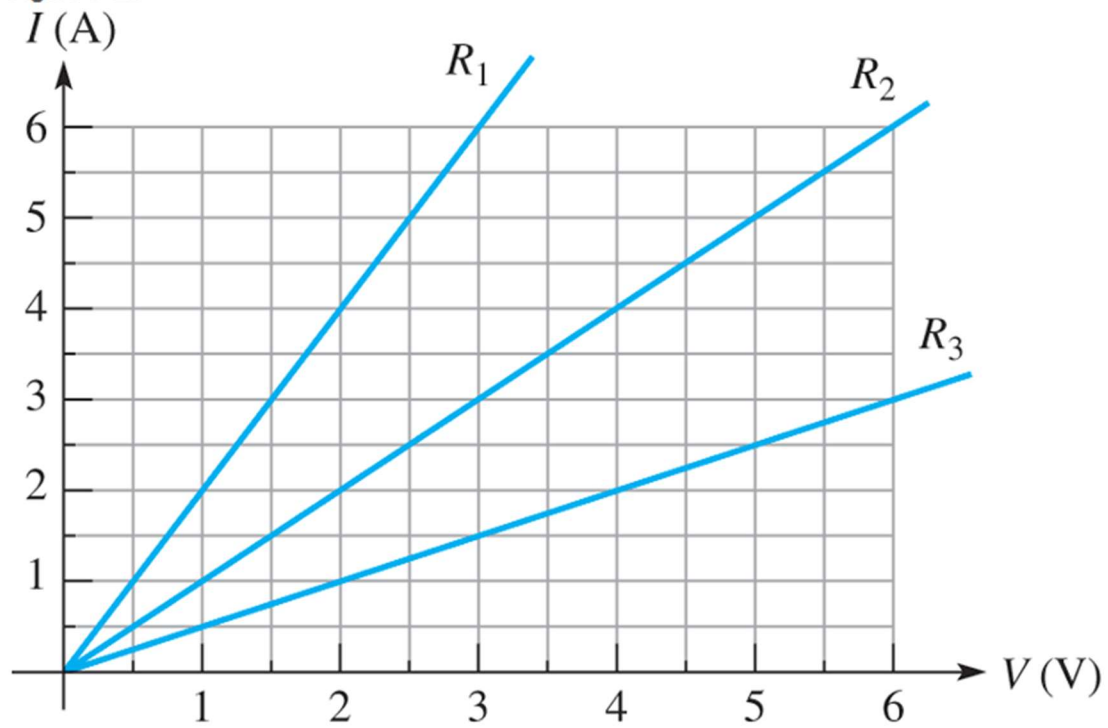

$$\frac{v}{i} = R$$

R1	$\frac{1}{2}, \frac{2}{4}$	$\frac{1}{2} \Omega$
R2	$\frac{1}{1}, \frac{2}{2}$	1Ω
R3	$\frac{2}{1}, \frac{4}{2}$	2Ω

Might be wire resistances

19. Assume 200 mV is across a **330 mΩ** current sensing resistor. What is the current through the resistor?

$$\frac{V}{R} = I$$

$$\frac{200 * 10^{-3}}{330 * 10^{-3}} = \frac{20}{33} = 0.606 \Omega$$