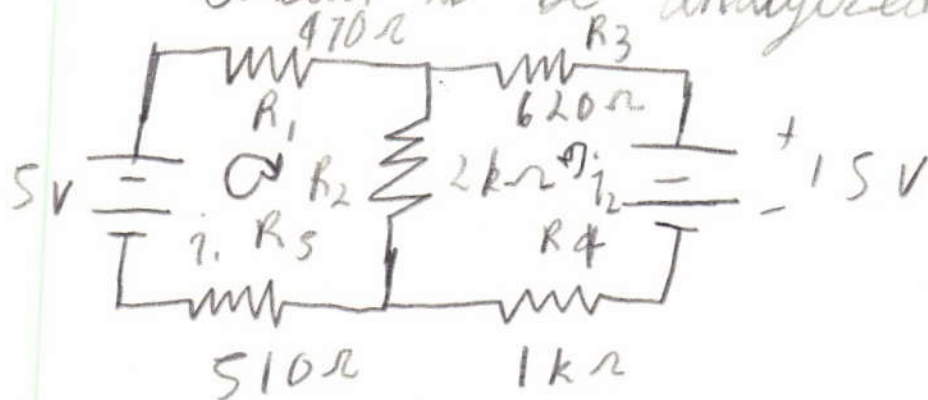



Objective: analysis of a two  
Source circuit via superposition  
theory claims that the effects on  
the circuit are the sum of the  
sources independent effects on the  
circuit.

Circuit to be analyzed:



theory says to compute one  
Source at a time to short  
voltage sources and break current  
Sources other than that of the  
one of analysis.

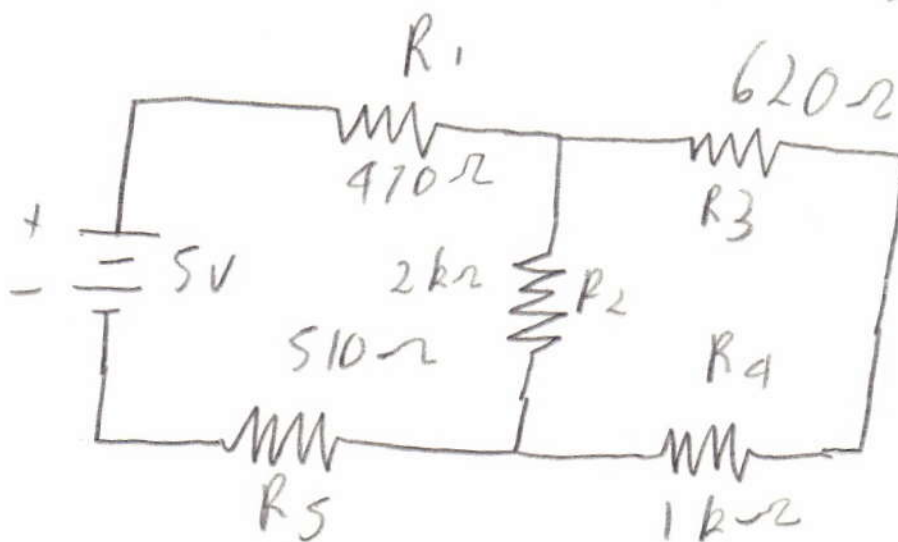first super position circuit  
5 V kept 15 volt shorted



seeking initial current converting  
to thevin equivalent

$$R_3 + R_4 = 1620 \Omega$$

$$R_{3+4} \parallel R_2 = \frac{1620 \times 2 \times 10^3}{1620 + 2000}$$

$$R_{3+4} \parallel R_2 = \frac{3240 \times 10^3}{3620}$$


$$R_{3+4 \parallel 2} = 895.027 \Omega$$

$$R_1 + R_{3+4 \parallel 2} + R_5 = 470 + 895.027 + 510$$

$$R_{Th \text{ circuit}_1} = 1875.027 \Omega$$

$$V_{Th} = I_{Th} R_{Th}$$

$$\frac{V_{Th}}{R_{Th}} = I_{Th}$$

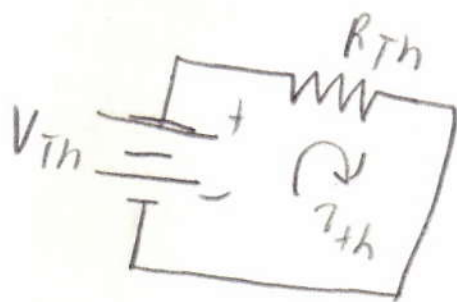

$$\frac{5}{1875.027} = 2.666 \text{ mA}$$

Initial current is 2.666 mA

Current divider at  $R_2$  and  $R_3 + R_4$

Current at  $R_5$  is known since exit current is equal to entry current from lab 4.

Current divider formula default

$$i_{\text{target}} = \frac{R_{\text{other}}}{\sum R} i_{\text{source}}$$

Current  $i_{R_2 \text{ circuit}_1}$

$$i_{R_2 \text{ circuit}_1} = \frac{620 + 1000}{1000 + 620 + 2000} 2.666 \times 10^{-3}$$

$$i_{R_2 \text{ circuit}_1} = \frac{1620}{3620} 2.666 \times 10^{-3}$$


$$i_{R_2 \text{ circuit}_1} = 1.193 \text{ mA}$$

Current  $i_{R_3+4}$  circuit 1

$$i_{R_3+4 \text{ circuit } 1} = \frac{2000}{1000 + 2000 + 620} \cdot 2.666 \times 10^{-3}$$

$$i_{R_3+4 \text{ circuit } 1} = 1.472 \text{ mA}$$

## Superposition circuit<sub>2</sub>

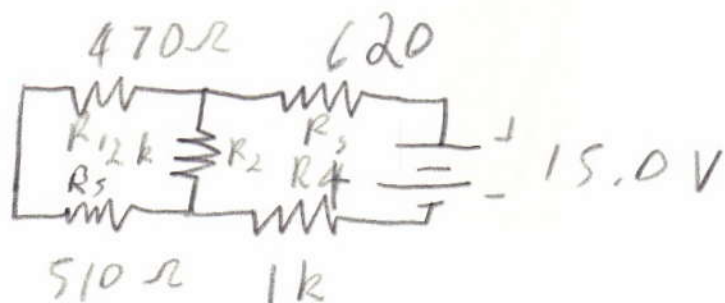

Theremin to find  $i_{th}$  or initial current and exit current.

$$R_1 + R_5 = 470 + 510 = 980 \Omega = R_{4+5}$$


$$R_{4+5} \parallel R_2 = \frac{980 \times 2000}{980 + 2000}$$

$$R_{4+5 \parallel 2} = 657.718 \Omega$$

$$R_{Th} = R_{4+5 \parallel 2} + R_3 + R_4 =$$

$$R_{th} = 657.718 + 620 + 1000 = 2277.718 \Omega$$

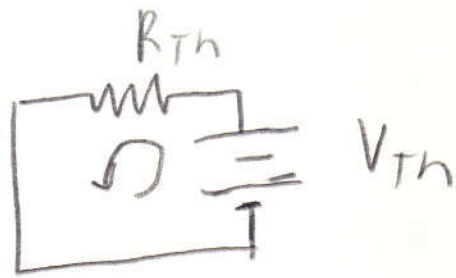Thevenin Superposition circuit<sub>2</sub>



$$i_{Th} = \frac{V_{Th}}{R_{Th}}$$


$$i_{Th \text{ circuit } 2} = \frac{15}{2277.718}$$

$$i_{Th \text{ circuit } 2} = 6.585 \text{ mA}$$

This is expected due to the higher voltage pushing more amps.



Current divider Superposition circuit 2.

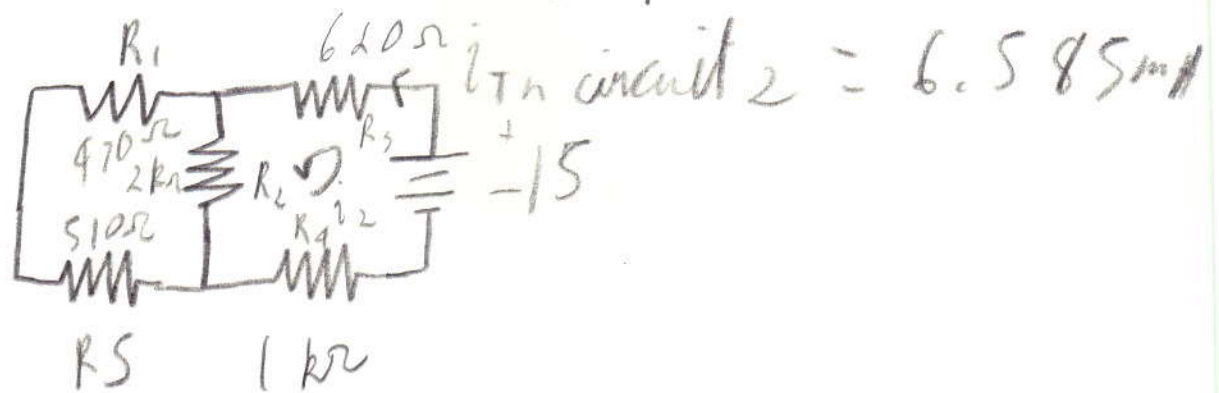

$$i_T = \frac{R_{\text{other}}}{\Sigma R} i_{\text{source}}$$

$$\Sigma R = R_1 + R_5 + R_4$$

$$\Sigma R = 470 + 510 + 2000$$

$$\Sigma R = 2980$$

$$R_{\text{other } R_2} = 980 \Omega = R_1 + R_5$$

$$R_{\text{other } R_1 + R_5} = 2000 \Omega$$


$$i_{R_2} = \frac{980}{2980} 6.585 \text{ mA}$$

$$i_{R_2} = 2.165 \text{ mA}$$

$$i_{R_1+R_5} = \frac{2600}{2980} 6.585 \text{ mA}$$

$$i_{R_1+R_5} = 4.419 \text{ mA}$$

Sum of currents original circuit.

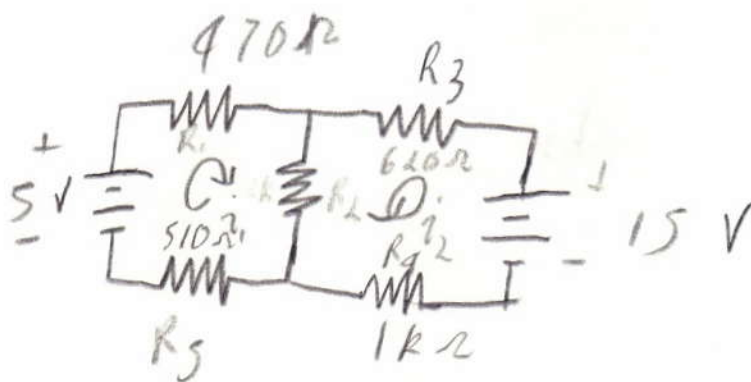

calculated currents

	5 V contribution	15 V contribution
$i_{R_1}$	2.666 mA	9.419 mA
$i_{R_2}$	1.193 mA	2.165 mA
$i_{R_3}$	1.472 mA	6.585 mA
$i_{R_4}$	1.472 mA	6.585 mA
$i_{R_5}$	2.666 mA	4.419 mA

analysis of direction

$i_{R_2}$  is summed

$i$  often are opposing

$\Sigma$  currents

$$i_{R_1} = (2.666 - 4.419) \text{ mA}$$

$$i_{R_1} = -1.753 \text{ mA}$$

$$i_{R_2} = (1.193 + 2.165) \text{ mA}$$

$$i_{R_2} = 3.358 \text{ mA}$$

$$i_{R3} = (-1.472 + 6.585) \text{ mA}$$

$$i_{R3} = 5.113 \text{ mA}$$

$$i_{R4} = (-1.472 + 6.585) \text{ mA}$$

$$i_{R4} = 5.113 \text{ mA}$$

$$i_{R5} = (-4.419 + 2.666) \text{ mA}$$

$$i_{R5} = -1.753 \text{ mA}$$

net currents

$i_{R1}$	$-1.753 \text{ mA}$
$i_{R2}$	$3.358 \text{ mA}$
$i_{R3}$	$5.113 \text{ mA}$
$i_{R4}$	$5.113 \text{ mA}$
$i_{R5}$	$-1.753 \text{ mA}$