

## CPE 1140

### 1. LAB NUMBER:

2

### 2. TITLE:

Series DC Circuit Analysis.

### 3. OBJECTIVES:

After completing this lab, the student will be able to:

- a) measure total resistance of a series circuit,
- b) measure total current supplied by a DC source,
- c) measure the voltage drop across each resistor of the circuit,
- d) verify Kirchhoff's Voltage Law,
- e) verify the Voltage Divider rule
- f) verify basic properties of a Series Circuit:
  - I. There is a single current following in a Series Circuit.
  - II. Resistor locations can be interchanged without affecting the value of the source current and the voltage drops.

### 4. EQUIPMENT:

DC Power Supply: Uni PS-2303  
Digital Multimeter: RIGOL DM 3058E  
Experimenter board (C.A.D.E.T.) or a Breadboard  
Multisim Software

### 5. COMPONENTS:

- 1 - 470  $\Omega$  ½ watt 5% Resistor
- 1 - 620  $\Omega$  ½ watt 5% Resistor
- 1 - 1000  $\Omega$  ½ watt 5% Resistor

### 6. TEXT REFERENCE:

Circuit Analysis: Theory and Practice (5<sup>th</sup> Edition):  
A.H. Robbins and W.C. Miller

Section 2.6: Measuring Voltage and Current  
Section 3.7: Measuring Resistance – the Ohmmeter  
Section 4.1: Ohm's Law  
Section 4.3: Power  
Chapter 5: Series Circuits

## 7. PRE-LAB ASSIGNMENT:

Study the series circuit in Figure 1 and do the followings:

Figure 1:

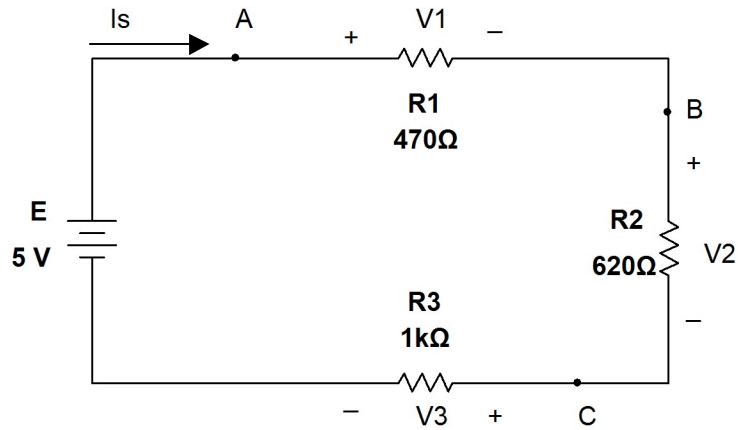


Table 1:

Resistor	Voltage Drop across R (volt)
R1: $470\Omega$	$V1 = 1.124$
R2: $620\Omega$	$V2 = 1.483$
R3: $1000\Omega$	$V3 = 2.392$

$R_t = 2090.000\Omega$
$I_s = 2.000\text{mA}$

- a) Calculate the total Resistance ( $R_t = R_1 + R_2 + R_3$ ). Record your result in Table 1.

$$R_{\text{total}} = \sum R_i = R_1 + R_2 + R_3 = 470 + 620 + 1000 = 2090.000$$

```
void sum_of_resistors()
```

```
{
```

```
    double set_of_resistors [] = {470.0,
```

```
                                   620.0,
```

```
                                   1000.0},
```

```
    series_of_resistors = 0.0;
```

```
    for(int count = 0; count < 3 ; count++)
```


```
    {
```

```
        series_of_resistors += set_of_resistors[count];
```

```
    }
```

```
    printf("The the sum of resisitors are : %.3lf\n",series_of_resistors);
```

```
}
```

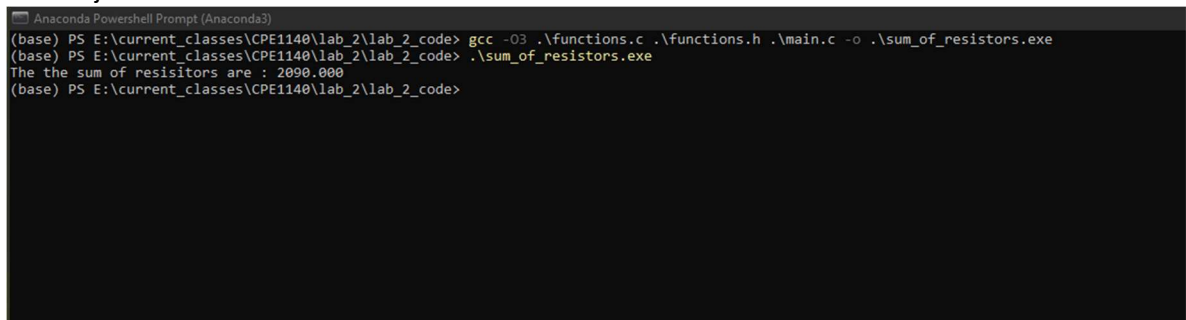

```
Anaconda PowerShell Prompt (Anaconda3)
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code> gcc -O3 .\functions.c .\functions.h .\main.c -o .\sum_of_resistors.exe
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code> .\sum_of_resistors.exe
The the sum of resisitors are : 2090.000
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code>
```

b) Calculate the source current  $I_s$  using Ohm's Law  $I_s = E/R_t$ .

Record your result in Table 1.

$$V=IR$$

$$V/R = I$$

$$I = 0.002 \text{ amps} * 10^3 * 10^{-3}$$

$$I = 2.000 \text{ miliAmps}$$

```
void source_current_series()
{
    double value_of_sum_of_resistors = 2090.000,
           source_voltage = 5.0,
           expected_current = 0.0;

    //v=iR
    //v/R = i
    expected_current = source_voltage / value_of_sum_of_resistors;
    printf("The expected current is about :%.3lf \n", expected_current);
}
```

```
Anaconda Powershell Prompt (Anaconda3)
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code> gcc -O3 .\functions.c .\functions.h .\main.c -o source_current_series
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code> .\source_current_series.exe
The expected current is about :0.002
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code> 0.002*1000
2
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code>
```

c) Calculate the Voltage Drop across each resistor using the Voltage Divider Rule:

$$V_x = \frac{R_x}{R_t} E$$

Record your results in Table 1.

$$V_{470 \text{ ohm}} = \frac{470}{2090} 5.0 = 1.124 \text{ volts}$$

$$V_{620 \text{ ohm}} = \frac{620}{2090} 5.0 = 1.483 \text{ volts}$$

$$V_{1000 \text{ ohm}} = \frac{1000}{2090} 5.0 = 2.392 \text{ volts}$$

```
void voltage_divder()
```

```
{
```

```
    double set_of_resistors [] = {470.0,  
                                   620.0,  
                                   1000.0},
```

```
    series_of_resistors = 2090,
```

```
    source_voltage = 5.0,
```

```
    voltage_target_resistor = 0.0;
```

```
    for (int count = 0 ; count < 3 ; count++ )
```

```
    {
```

```
        voltage_target_resistor = source_voltage *
```

```
set_of_resistors[count]/series_of_resistors;
```

```
        printf("the expected voltage of %.3lf ohm resistors is about %.3lf volts \n",
```

```
            set_of_resistors[count], voltage_target_resistor
```

```
        );
```

```
    }
```

```
}
```

```
Anaconda PowerShell Prompt (Anaconda3)
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code> gcc -O2 .\functions.c .\functions.h .\main.c -o voltage_divider
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code> .\voltage_divider.exe
the expected voltage of 470.000 ohm resistors is about 1.124 volts
the expected voltage of 620.000 ohm resistors is about 1.483 volts
the expected voltage of 1000.000 ohm resistors is about 2.392 volts
(base) PS E:\current_classes\CPE1140\lab_2\lab_2_code>
```

## 8. MEASUREMENTS:

### A – Resistance Measurement:

- Connect  $R_1$ ,  $R_2$ ,  $R_3$  in series on the experimenter board as in Fig.1 without the source E.2.
- Set the DMM to measure Resistance ( $\Omega$ ). Measure the total resistance of this circuit ( $R_{123}$ ). Record your result in the following Table 2:

Table 2:

$R_{123} =$	$\Omega$
$R_{321} =$	$\Omega$

- Interchange the location of  $R_1$  ( $470\ \Omega$ ) and  $R_3$  ( $1K\Omega$ ). Measure the total resistance again ( $R_{321}$ ). Record your result in Table 2.
- Are the two results ( $R_{123}$  and  $R_{321}$ ) different?
- How are these results compared to the calculated  $R_t$  in Table 1? Is the difference within the 5% tolerance of the resistors?

### B – Source Current Measurement:

- Locate the **fixed 5V** source on the power supply. Connect this source to the 3 resistors in series ( $R_3$ ,  $R_2$ ,  $R_1$ ). Set the DMM to measure DC voltage and measure the source voltage. Record your result in Table 3:

Table 3:

Source E =	V
$I_{321}(A) =$	mA
$I_{123}(A) =$	mA
$I_{123}(B) =$	mA
$I_{123}(C) =$	mA

Note: The current subscript reflects the resistor sequence in the circuit.

- Set the DMM to measure DC current and measure the source current  $I_{321}$  at location **A**. Record your result in Table 3.
- Interchange the locations of resistors  $R_1$  and  $R_3$  (the sequence is now  $R_1$ - $R_2$ - $R_3$ ). Measure the source current  $I_{123}$  at location **A**. Record your result in Table 3.
- Measure the source current  $I_{123}$  at locations **B** and **C**. Record your result in Table 3.
- Compare these results of source current to  $I_s$  in Table 1:
  - Are they within the 5% tolerance of the resistors?
  - Did the location of measurement of current affect the values?
  - Did the interchange of Resistors affect the values of the currents?

### C- Voltage Drop Measurement:

- k) Set the DMM to measure DC voltage and measure the voltage drops across each resistor (see Fig. 1). Pay attention to the placement of the probes so that all voltage readings are positive. Record your results in Table 4:

Table 4:

Voltage Drop across R (volt)
$V_1 =$
$V_2 =$
$V_3 =$
$V_t =$

- l) Calculate  $V_t = V_1 + V_2 + V_3$  and record your result in Table 4.  
m) Compare the results of Table 4 to those of Table 1. Compare  $V_t$  to E in Table 3.

### D- Multisim Simulations:

- n) Create a Multisim circuit (similar to Fig.1) with the followings:
1. One Voltmeter measures the source voltage E and 3 Voltmeters measure  $V_1$ ,  $V_2$ ,  $V_3$ .
  2. Three Ammeters measure source current at A, B and C.

## 9. LAB-REPORT REQUIREMENT:

Your team's Lab Report should contain the followings:

**A Cover Page** with Lab Number, Lab Title, Team members' Names and Date.

**Result Pages** with:

#### A- Resistance Measurement:

Results:

Show a copy of Table 2

Discussions:

1. Answer question in 8(d).
2. Answer question in 8(e).
3. What conclusion can you make about the locations of resistors in a series circuit

#### B- Source Current Measurement:

Results:

Show a copy of Table 3.

Discussions:

1. Answer questions in 8(j). Take also Multisim currents in consideration.
2. What conclusion can you make about the effect of location on the measurement of source current in a series circuit?

### C- Voltage Drop Measurement:

#### Results:

Show a copy of Table 4.

#### Discussions:

1. Make the comparisons in 8(m). Take also Multisim voltages in consideration.
2. From the results of Table 4, what conclusion can you make about the Voltage Divider Rule

### D- Power Study:

#### Results:

With the data in Table 1, calculate the Powers dissipated in  $R_1$ ,  $R_2$  and  $R_3$ , using the formula  $P = I^2 R$ . Record your results in Table 5.

Table 5:

Resistor	Power dissipated (W)
$R_1$	$P_1 =$
$R_2$	$P_2 =$
$R_3$	$P_3 =$

#### Discussions:

With the above results, discuss if the “1/2 watts” rating of the resistors is suitable for this lab.

### E- Conclusion: *(it helps to compare your prelab with measured results)*

1. Did the above results demonstrate the validity of Kirchhoff's Voltage Law? Explain your answer.
2. Is the Voltage Divider Rule accurate? Explain your answer.
3. Are all the Lab objectives met? Explain if some are not.

**Appendix:** Attach a printout of **Multisim** simulation and all **Pre-Lab** calculations.